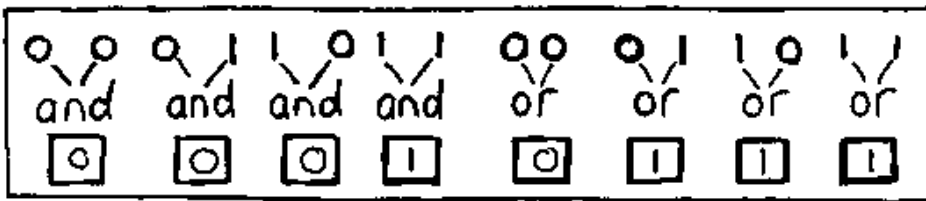
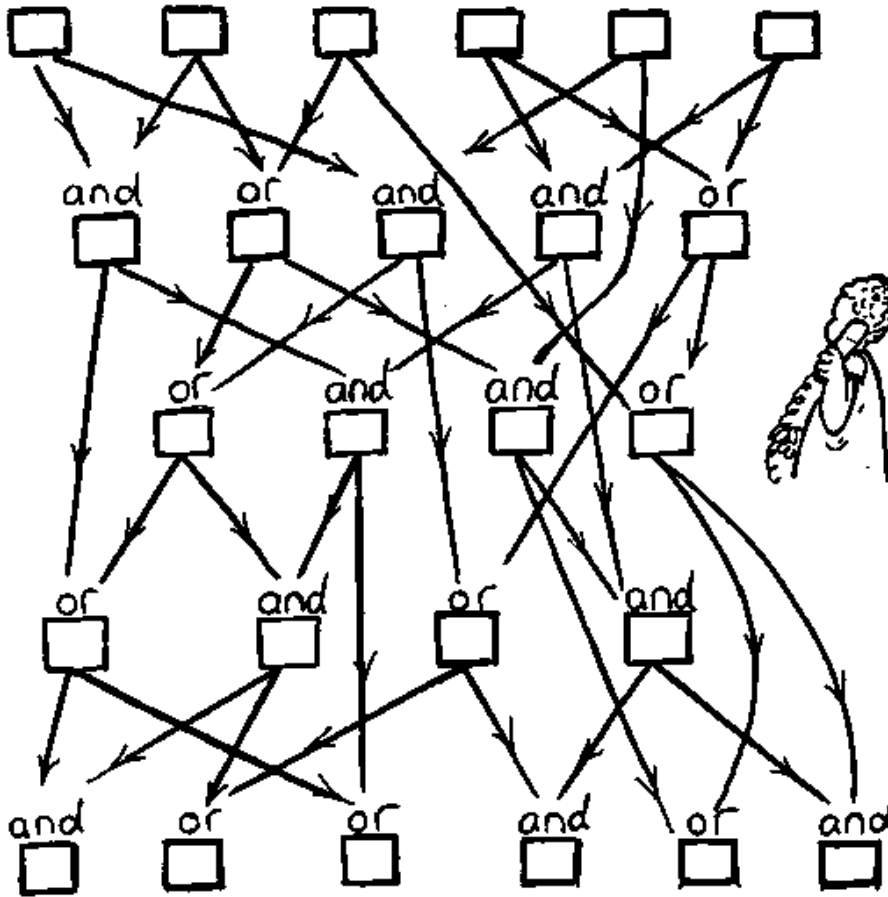




KEY □ = **1** = true
 □ = ● = false



Instructions: Choose some inputs for this circuit and work out what the outputs are.